


Lecture 14: Sequential Circuits, FSM

- Today's topics:
 - Adder wrap-up
 - Sequential circuits
 - Finite state machines

Adder Summary

- Using the generate/propagate abstraction to add layers of ccts
- Key: all g/p/G/P signals can be calculated based on a/b inputs (they don't need carry-in as inputs, so they can all be done rightaway in parallel)
- First calculate g/p with 1 gate delay: $g_i = a_i \cdot b_i$; $p_i = a_i + b_i$
- Then calculate G/P with up to 2 gate delays (for a block of 4 bits):
 $G_i = g_3 + g_2 \cdot p_3 + g_1 \cdot p_2 \cdot p_3 + g_0 \cdot p_1 \cdot p_2 \cdot p_3$
 $P_i = p_0 \cdot p_1 \cdot p_2 \cdot p_3$
- Then calculate all the carries, including for the 16th bit, with 2 more gate delays:
 $C_4 = G_3 + (P_3 \cdot G_2) + (P_3 \cdot P_2 \cdot G_1) + (P_3 \cdot P_2 \cdot P_1 \cdot G_0) + (P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot c_0)$
- Thus, this abstraction enables a design with a modest number of total gates, a modest number of delays, and a modest number of inputs per gate.

Trade-Off Curve

 


Clocks

- A microprocessor is composed of many different circuits that are operating simultaneously – if each circuit X takes in inputs at time TI_x , takes time TE_x to execute the logic, and produces outputs at time TO_x , imagine the complications in co-ordinating the tasks of every circuit
- A major school of thought (used in most processors built today): all circuits on the chip share a clock signal (a square wave) that tells every circuit when to accept inputs, how much time they have to execute the logic, and when they must produce outputs




Clock Terminology

 


$$4 \text{ GHz} = \text{clock speed} = \frac{1}{\text{cycle time}} = \frac{1}{250 \text{ ps}}.$$

Sequential Circuits

 - Until now, circuits were combinational – when inputs change, the outputs change after a while (time = logic delay thru circuit)




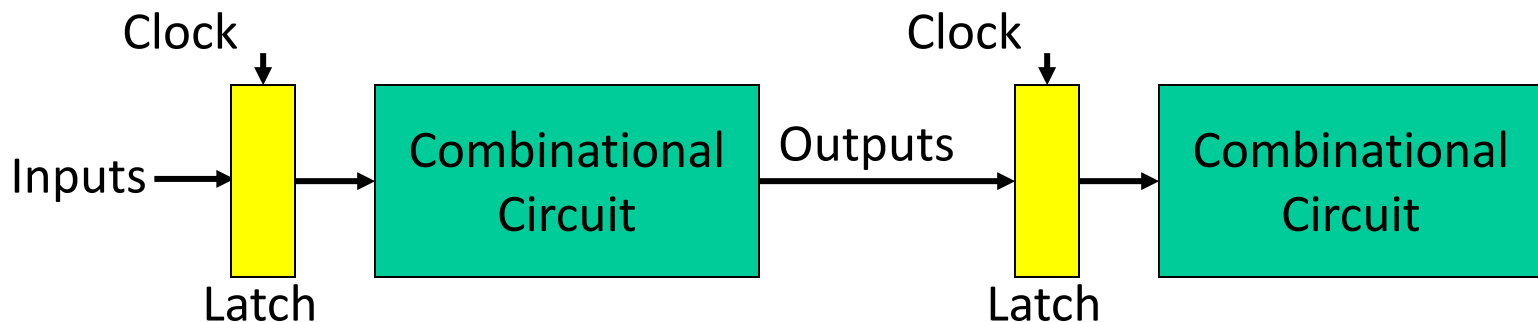- We want the clock to act like a start and stop signal – a “latch” is a storage device that separates these circuits – it ensures that the inputs to the circuit do not change during a clock cycle



Sequential Circuits

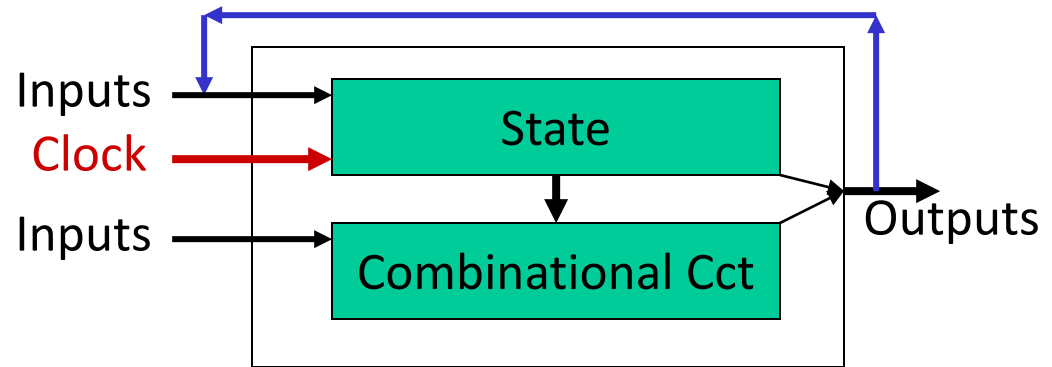- Sequential circuit: consists of combinational circuit and a storage element
- At the start of the clock cycle, the rising edge causes the “state” storage to store some input values




- This state will not change for an entire cycle (until next rising edge)
- The combinational circuit has some time to accept the value of “state” and “inputs” and produce “outputs”
- Some of the outputs (for example, the value of next “state”) may feed back (but through the latch so they’re only seen in the next cycle)

Designing a Latch


- An S-R latch: set-reset latch
 - When Set is high, a 1 is stored
 - When Reset is high, a 0 is stored
 - When both are low, the previous state is preserved (hence, known as a storage or memory element)
 - Both are high – this set of inputs is not allowed

Verify the above behavior!

 


D Latch

 - Incorporates a clock
- The value of the input D signal (data) is stored only when the clock is high – the previous state is preserved when the clock is low




D Flip Flop

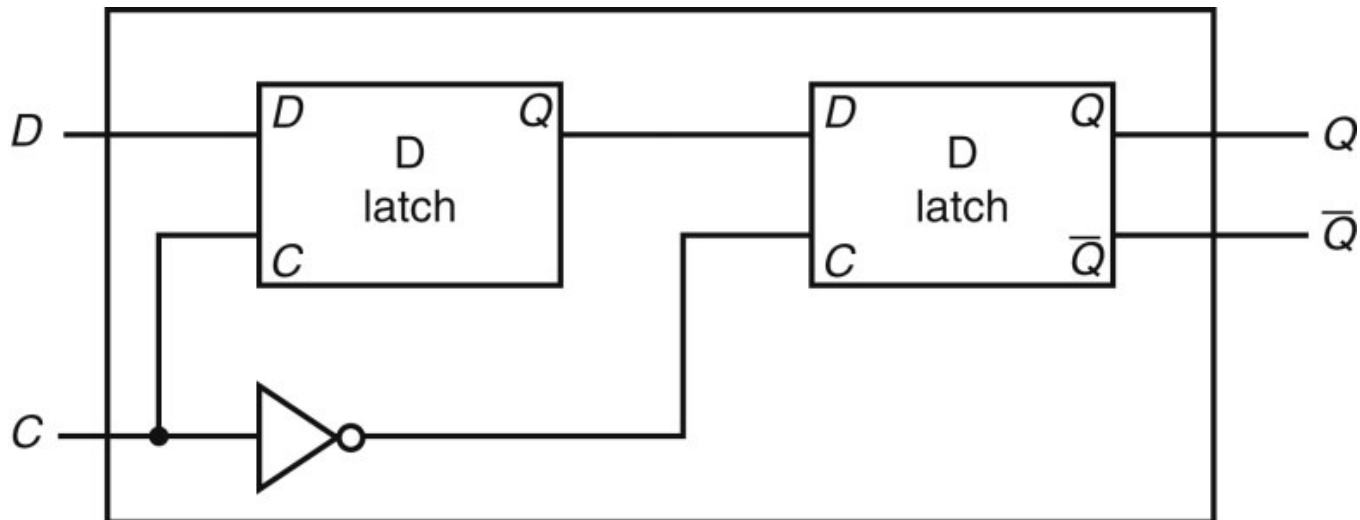- Terminology:
Latch: outputs can change any time the clock is high (asserted)
Flip flop: outputs can change only on a clock edge
- Two D latches in series – ensures that a value is stored only on the falling edge of the clock




Finite State Machine

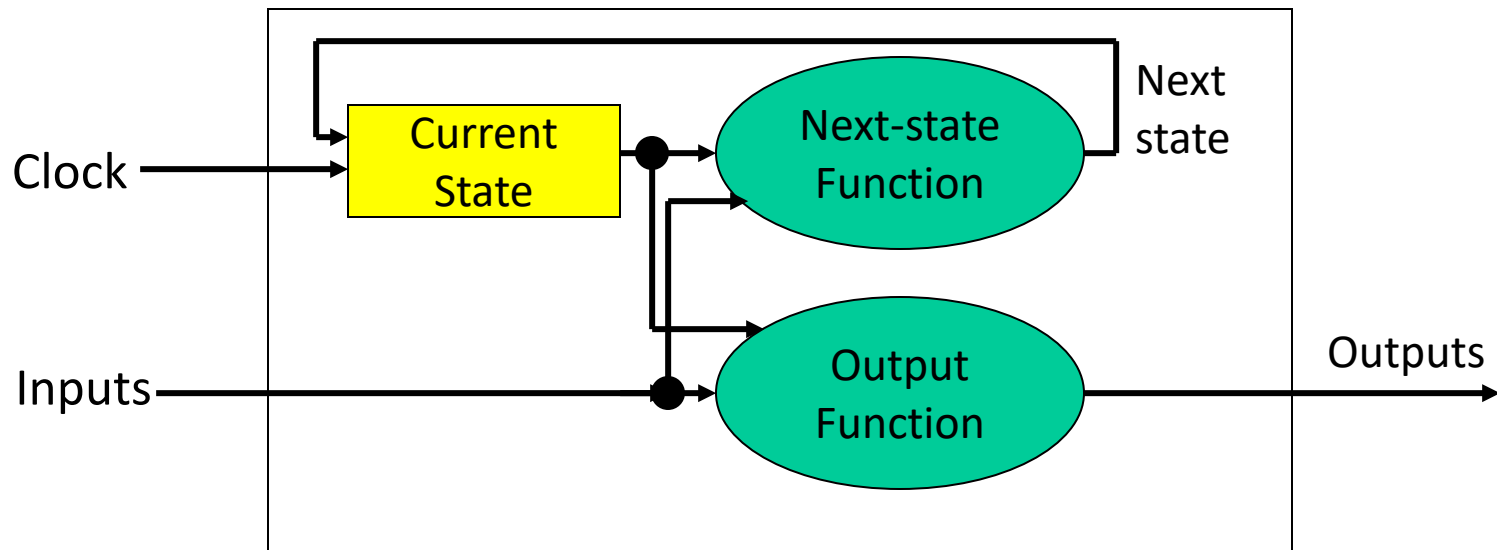- A sequential circuit is described by a variation of a truth table – a finite state diagram (hence, the circuit is also called a finite state machine)
- Note that state is updated only on a clock edge



State Diagrams

 - Each state is shown with a circle, labeled with the state value – the contents of the circle are the outputs
- An arc represents a transition to a different state, with the inputs indicated on the label



This is a state diagram for ____?

3-Bit Counter

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:


- How many states?
- How many inputs?

3-Bit Counter

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:

- How many states?
- How many inputs?

 

Tackling FSM Problems

- Three questions worth asking:
 - What are the possible output states? Draw a bubble for each.
 - What are inputs? What values can those inputs take?
 - For each state, what do I do for each possible input value? Draw an arc out of every bubble for every input value.

Traffic Light Controller

- Problem description: A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red); there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light need change only if a car is waiting on the other road

State Transition Table:

How many states?

How many inputs?

How many outputs?

State Transition Table

- Problem description: A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red); there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light must change only if a car is waiting on the other road


State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

State Diagram

State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

 

Source: H&P textbook

Tackling FSM Problems

- Three questions worth asking:
 - What are the possible output states? Draw a bubble for each.
 - What are inputs? What values can those inputs take?
 - For each state, what do I do for each possible input value? Draw an arc out of every bubble for every input value.


Example – Residential Thermostat

- Two temp sensors: internal and external
- If internal temp is within 1 degree of desired, don't change setting
- If internal temp is > 1 degree higher than desired, turn AC on; if internal temp is < 1 degree lower than desired, turn heater on
- If external temp and desired temp are within 5 degrees, disregard the internal temp, and turn both AC and heater off

Finite State Machine Table

Current State	Input E	Input I	Output State
HEAT	D	C	OFF
HEAT	D	G	OFF
HEAT	D	H	OFF
HEAT	U	C	HEAT
HEAT	U	G	HEAT
HEAT	U	H	COOL
COOL	D	C	OFF
COOL	D	G	OFF
COOL	D	H	OFF
COOL	U	C	HEAT
COOL	U	G	COOL
COOL	U	H	COOL
OFF	D	C	OFF
OFF	D	G	OFF
OFF	D	H	OFF
OFF	U	C	HEAT
OFF	U	G	OFF
OFF	U	H	COOL

Finite State Diagram

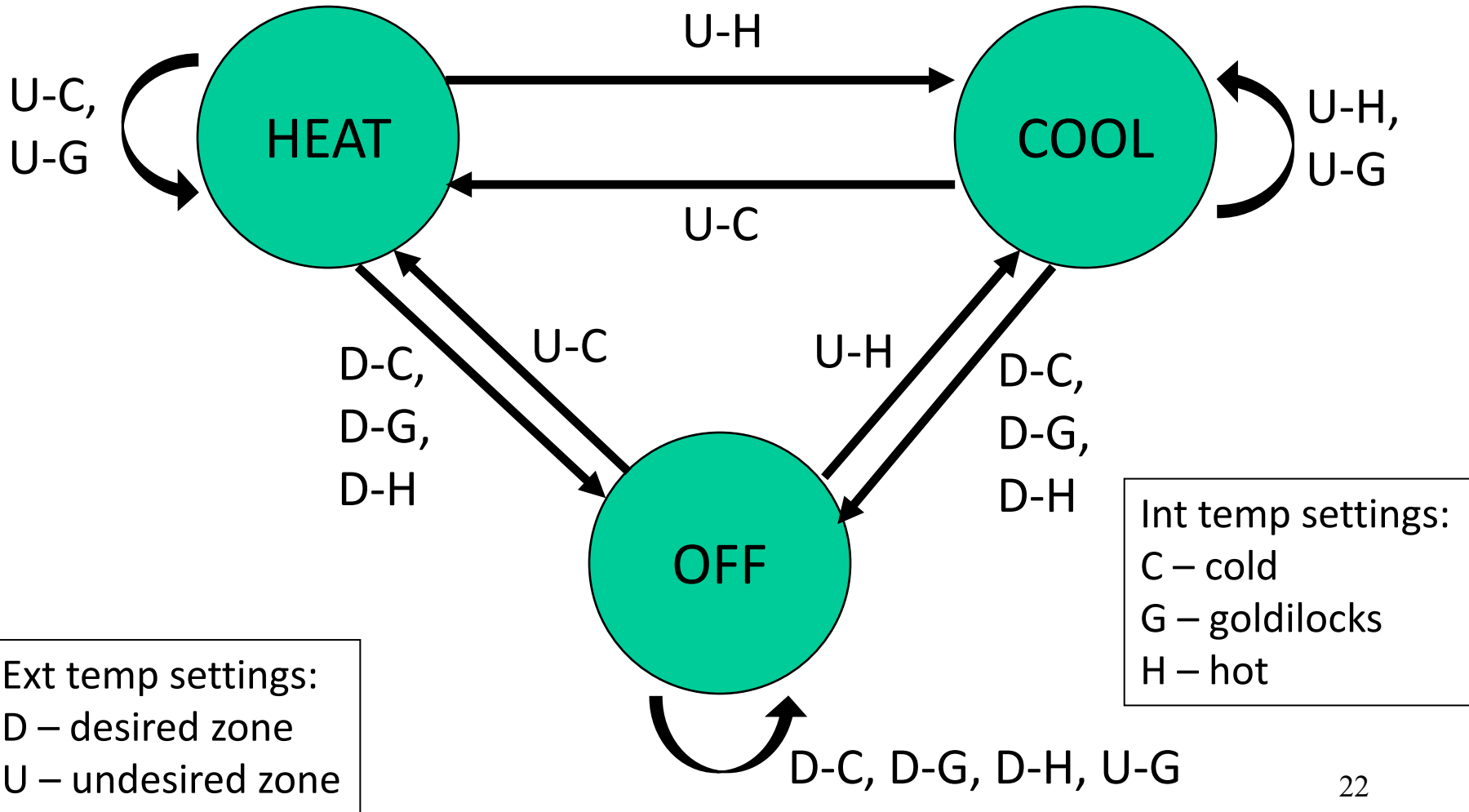

Latch vs. Flip-Flop

- Recall that we want a circuit to have stable inputs for an entire cycle – so I want my new inputs to arrive at the start of a cycle and be fixed for an entire cycle
- A flip-flop provides the above semantics (a door that swings open and shut at the start of a cycle)
- But a flip-flop needs two back-to-back D-latches, i.e., more transistors, delay, power
- You can reduce these overheads with just a single D-latch (a door that is open for half a cycle) as long as you can tolerate stable inputs for just half a cycle