

Lecture 13: Sequential Circuits

- Today's topics:
 - Carry-lookahead adder
 - Clocks and sequential circuits
 - Finite state machines
- Reminder: Assignment 5 due on Thursday 10/12, mid-term exam Tuesday 10/24

Speed of Ripple Carry

- The carry propagates thru every 1-bit box: each 1-bit box sequentially implements AND and OR – total delay is the time to go through 64 gates!
- We've already seen that any logic equation can be expressed as the sum of products – so it should be possible to compute the result by going through only 2 gates!
- Caveat: need many parallel gates and each gate may have a very large number of inputs – it is difficult to efficiently build such large gates, so we'll find a compromise:
 - moderate number of gates
 - moderate number of inputs to each gate
 - moderate number of sequential gates traversed

Computing CarryOut

$$\text{CarryIn1} = b0.\text{CarryIn0} + a0.\text{CarryIn0} + a0.b0$$

$$\begin{aligned}\text{CarryIn2} &= b1.\text{CarryIn1} + a1.\text{CarryIn1} + a1.b1 \\ &= b1.b0.c0 + b1.a0.c0 + b1.a0.b0 + \\ &\quad a1.b0.c0 + a1.a0.c0 + a1.a0.b0 + a1.b1\end{aligned}$$

...

CarryIn32 = a really large sum of really large products

- Potentially fast implementation as the result is computed by going thru just 2 levels of logic – unfortunately, each gate is enormous and slow

Generate and Propagate

Equation re-phrased:

$$\begin{aligned} c_{i+1} &= a_i.b_i + a_i.c_i + b_i.c_i \\ &= (a_i.b_i) + (a_i + b_i).c_i \end{aligned}$$

Stated verbally, the current pair of bits will *generate* a carry if they are both 1 and the current pair of bits will *propagate* a carry if either is 1

Generate signal = $a_i.b_i$

Propagate signal = $a_i + b_i$

Therefore, $c_{i+1} = g_i + p_i . c_i$

Generate and Propagate

$$c1 = g0 + p0.c0$$

$$c2 = g1 + p1.c1$$

$$= g1 + p1.g0 + p1.p0.c0$$

$$c3 = g2 + p2.g1 + p2.p1.g0 + p2.p1.p0.c0$$

$$c4 = g3 + p3.g2 + p3.p2.g1 + p3.p2.p1.g0 + p3.p2.p1.p0.c0$$

Either,

a carry was just generated, or


a carry was generated in the last step and was propagated, or

a carry was generated two steps back and was propagated by both the next two stages, or

a carry was generated N steps back and was propagated by every single one of the N next stages

Divide and Conquer

 - The equations on the previous slide are still difficult to implement as logic functions – for the 32nd bit, we must AND every single propagate bit to determine what becomes of c0 (among other things)
- Hence, the bits are broken into groups (of 4) and each group computes its group-generate and group-propagate
- For example, to add 32 numbers, you can partition the task as a tree



P and G for 4-bit Blocks

- Compute P0 and G0 (super-propagate and super-generate) for the first group of 4 bits (and similarly for other groups of 4 bits)

$$P0 = p0.p1.p2.p3$$

$$G0 = g3 + g2.p3 + g1.p2.p3 + g0.p1.p2.p3$$

- Carry out of the first group of 4 bits is

$$C1 = G0 + P0.c0$$

$$C2 = G1 + P1.G0 + P1.P0.c0$$

...

- By having a tree of sub-computations, each AND, OR gate has few inputs and logic signals have to travel through a modest set of gates (equal to the height of the tree)

Example

Add	A	0001	1010	0011	0011
and	B	1110	0101	1110	1011
		<hr/>			
	g	0000	0000	0010	0011
	p	1111	1111	1111	1011

P	1	1	1	0
G	0	0	1	0

C4 = 1

Carry Look-Ahead Adder

- 16-bit Ripple-carry takes 32 steps
- This design takes how many steps?

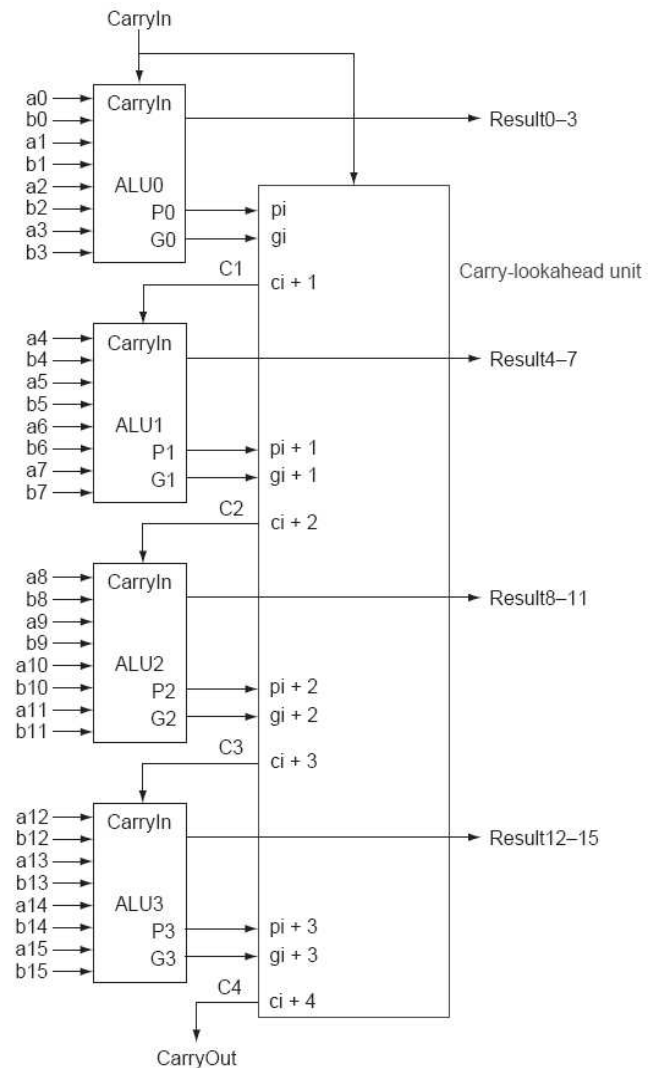



FIGURE B.6.3 Four 4-bit ALUs using carry lookahead to form a 16-bit adder. Note that the carries come from the carry-lookahead unit, not from the 4-bit ALUs.

Clocks

- A microprocessor is composed of many different circuits that are operating simultaneously – if each circuit X takes in inputs at time TI_X , takes time TE_X to execute the logic, and produces outputs at time TO_X , imagine the complications in co-ordinating the tasks of every circuit
- A major school of thought (used in most processors built today): all circuits on the chip share a clock signal (a square wave) that tells every circuit when to accept inputs, how much time they have to execute the logic, and when they must produce outputs




Clock Terminology

 


$$4 \text{ GHz} = \text{clock speed} = \frac{1}{\text{cycle time}} = \frac{1}{250 \text{ ps}}.$$

Sequential Circuits

 - Until now, circuits were combinational – when inputs change, the outputs change after a while (time = logic delay thru circuit)




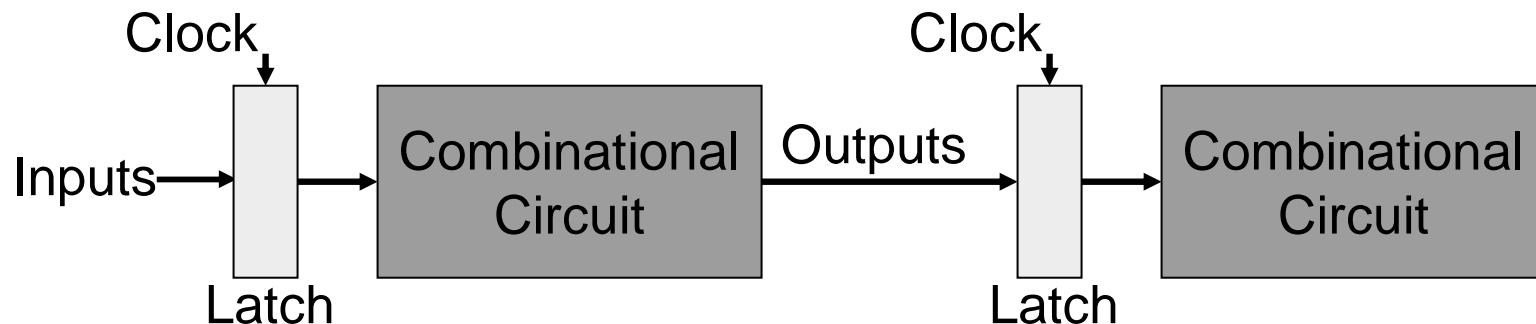- We want the clock to act like a start and stop signal – a “latch” is a storage device that stores its inputs at a rising clock edge and this storage will not change until the next rising clock edge



Sequential Circuits

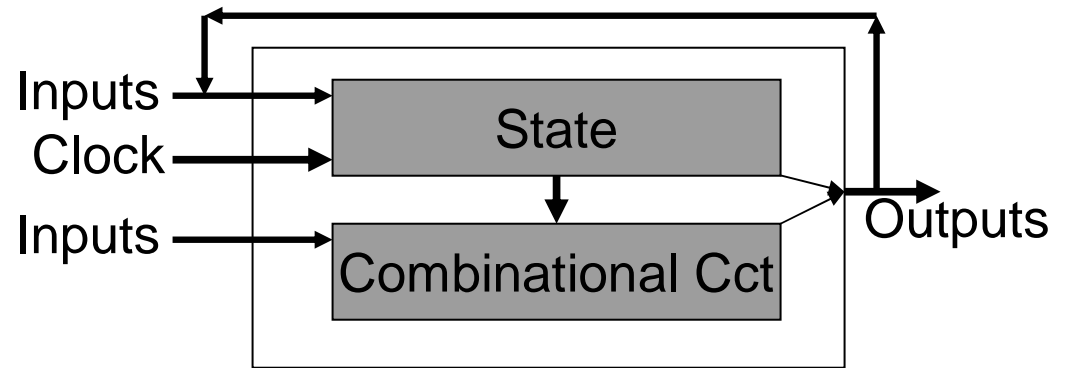- Sequential circuit: consists of combinational circuit and a storage element
- At the start of the clock cycle, the rising edge causes the “state” storage to store some input values




- This state will not change for an entire cycle (until next rising edge)
- The combinational circuit has some time to accept the value of “state” and “inputs” and produce “outputs”
- Some of the outputs (for example, the value of next “state”) may feed back (but through the latch so they’re only seen in the next cycle)

Designing a Latch


- An S-R latch: set-reset latch
 - When Set is high, a 1 is stored
 - When Reset is high, a 0 is stored
 - When both are low, the previous state is preserved (hence, known as a storage or memory element)
 - When both are high, the output is unstable – this set of inputs is therefore not allowed

Verify the above behavior!

 


D Latch

 - Incorporates a clock
- The value of the input D signal (data) is stored only when the clock is high – the previous state is preserved when the clock is low




D Flip Flop

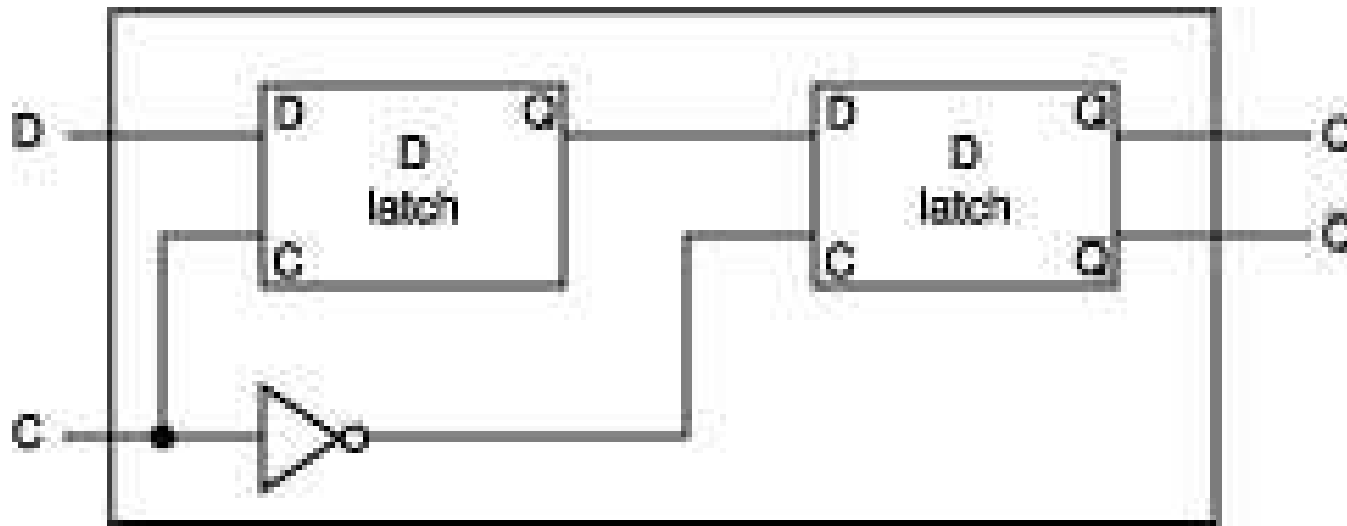- Terminology:
Latch: outputs can change any time the clock is high (asserted)
Flip flop: outputs can change only on a clock edge
- Two D latches in series – ensures that a value is stored only on the falling edge of the clock




Sequential Circuits

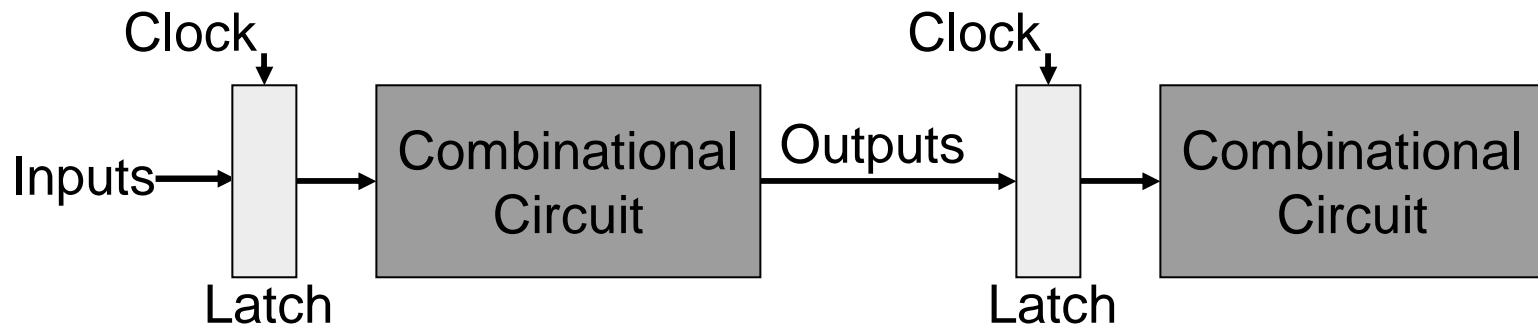- We want the clock to act like a start and stop signal – a “latch” is a storage device that stores its inputs at a rising clock edge and this storage will not change until the next rising clock edge




Finite State Machine

 - A sequential circuit is described by a variation of a truth table – a finite state diagram (hence, the circuit is also called a finite state machine)
- Note that state is updated only on a clock edge



State Diagrams

 - Each state is shown with a circle, labeled with the state value – the contents of the circle are the outputs
- An arc represents a transition to a different state, with the inputs indicated on the label



This is a state diagram for ____?

3-Bit Counter

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:


- How many states?
- How many inputs?

3-Bit Counter

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:

- How many states?
- How many inputs?

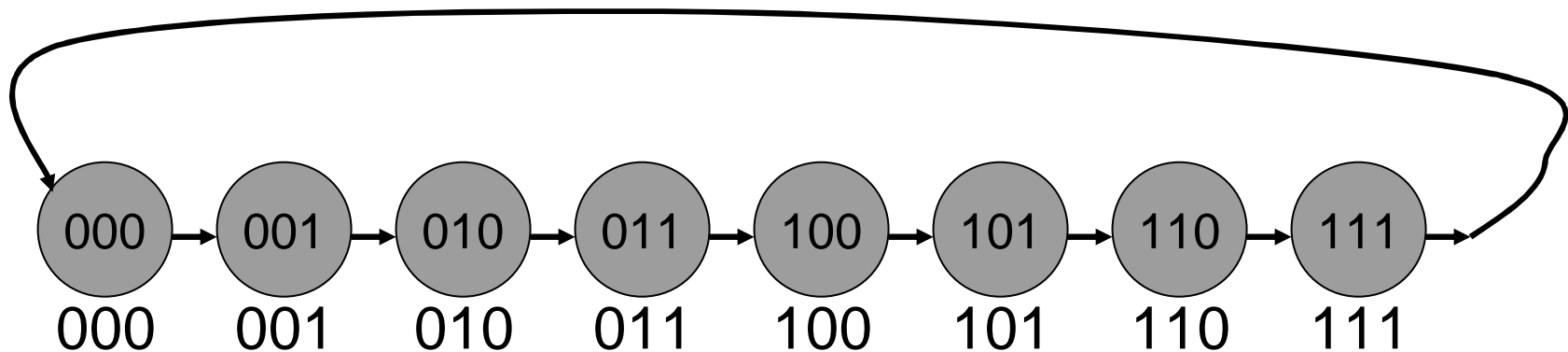

Traffic Light Controller

- Problem description: A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red); there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light need change only if a car is waiting on the other road

State Transition Table:

How many states?

How many inputs?

How many outputs?

State Transition Table

- Problem description: A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red); there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light must change only if a car is waiting on the other road


State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

State Diagram

State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

 

Title

- Bullet