


# Lecture 13: Adders, Sequential Circuits

---

- Today's topics:
  - Carry-lookahead adder
  - Clocks, latches, sequential circuits

 
# Incorporating slt

- Perform  $a - b$  and check the sign
- New signal (Less) that is zero for ALU boxes 1-31
- The 31<sup>st</sup> box has a unit to detect overflow and sign – the sign bit serves as the Less signal for the 0<sup>th</sup> box



 
# Incorporating beq

- Perform  $a - b$  and confirm that the result is all zero's


 
# Control Lines


What are the values of the control lines and what operations do they correspond to?



# Control Lines

What are the values of the control lines and what operations do they correspond to?

	Ai	Bn	Op
AND	0	0	00
OR	0	0	01
Add	0	0	10
Sub	0	1	10
SLT	0	1	11
NOR	1	1	00
NAND	1	1	01

 

# Speed of Ripple Carry

---

- The carry propagates thru every 1-bit box: each 1-bit box sequentially implements AND and OR – total delay is the time to go through 64 gates!
- We've already seen that any logic equation can be expressed as the sum of products – so it should be possible to compute the result by going through only 2 gates!
- Caveat: need many parallel gates and each gate may have a very large number of inputs – it is difficult to efficiently build such large gates, so we'll find a compromise:
  - moderate number of gates
  - moderate number of inputs to each gate
  - moderate number of sequential gates traversed

# Computing CarryOut

---

$$\text{CarryIn1} = b_0 \cdot \text{CarryIn0} + a_0 \cdot \text{CarryIn0} + a_0 \cdot b_0$$

$$\begin{aligned} \text{CarryIn2} &= b_1 \cdot \text{CarryIn1} + a_1 \cdot \text{CarryIn1} + a_1 \cdot b_1 \\ &= b_1 \cdot b_0 \cdot c_0 + b_1 \cdot a_0 \cdot c_0 + b_1 \cdot a_0 \cdot b_0 + \\ &\quad a_1 \cdot b_0 \cdot c_0 + a_1 \cdot a_0 \cdot c_0 + a_1 \cdot a_0 \cdot b_0 + a_1 \cdot b_1 \end{aligned}$$

...

$\text{CarryIn32}$  = a really large sum of really large products

- Potentially fast implementation as the result is computed by going thru just 2 levels of logic – unfortunately, each gate is enormous and slow

# Generate and Propagate

---

Equation re-phrased:

$$\begin{aligned} C_{i+1} &= a_i \cdot b_i + a_i \cdot C_i + b_i \cdot C_i \\ &= (a_i \cdot b_i) + (a_i + b_i) \cdot C_i \end{aligned}$$

Stated verbally, the current pair of bits will *generate* a carry if they are both 1 and the current pair of bits will *propagate* a carry if either is 1

Generate signal =  $a_i \cdot b_i$

Propagate signal =  $a_i + b_i$

Therefore,  $C_{i+1} = G_i + P_i \cdot C_i$

# Generate and Propagate

---

$$c1 = g0 + p0.c0$$

$$c2 = g1 + p1.c1$$

$$= g1 + p1.g0 + p1.p0.c0$$

$$c3 = g2 + p2.g1 + p2.p1.g0 + p2.p1.p0.c0$$

$$c4 = g3 + p3.g2 + p3.p2.g1 + p3.p2.p1.g0 + p3.p2.p1.p0.c0$$

Either,

a carry was just generated, or

a carry was generated in the last step and was propagated, or


a carry was generated two steps back and was propagated by both the next two stages, or

a carry was generated N steps back and was propagated by every single one of the N next stages
 
# Divide and Conquer

---

- The equations on the previous slide are still difficult to implement as logic functions – for the 32<sup>nd</sup> bit, we must AND every single propagate bit to determine what becomes of c0 (among other things)
- Hence, the bits are broken into groups (of 4) and each group computes its group-generate and group-propagate
- For example, to add 32 numbers, you can partition the task as a tree



# P and G for 4-bit Blocks

---

- Compute P0 and G0 (super-propagate and super-generate) for the first group of 4 bits (and similarly for other groups of 4 bits)  
$$P0 = p0.p1.p2.p3$$
$$G0 = g3 + g2.p3 + g1.p2.p3 + g0.p1.p2.p3$$
- Carry out of the first group of 4 bits is  
$$C1 = G0 + P0.c0$$
$$C2 = G1 + P1.G0 + P1.P0.c0$$
$$C3 = G2 + (P2.G1) + (P2.P1.G0) + (P2.P1.P0.c0)$$
$$C4 = G3 + (P3.G2) + (P3.P2.G1) + (P3.P2.P1.G0) + (P3.P2.P1.P0.c0)$$
- By having a tree of sub-computations, each AND, OR gate has few inputs and logic signals have to travel through a modest set of gates (equal to the height of the tree)

# Example

---


Add	A	0001	1010	0011	0011
	B	1110	0101	1110	1011
<hr/>					
	g	0000	0000	0010	0011
	p	1111	1111	1111	1011

P	1	1	1	0
G	0	0	1	0

C4 = 1
 
# Carry Look-Ahead Adder

- 16-bit Ripple-carry takes 32 steps
- This design takes how many steps?



# Clocks


---

- A microprocessor is composed of many different circuits that are operating simultaneously – if each circuit  $X$  takes in inputs at time  $TI_X$ , takes time  $TE_X$  to execute the logic, and produces outputs at time  $TO_X$ , imagine the complications in co-ordinating the tasks of every circuit
- A major school of thought (used in most processors built today): all circuits on the chip share a clock signal (a square wave) that tells every circuit when to accept inputs, how much time they have to execute the logic, and when they must produce outputs



# Clock Terminology

---

 


$$4 \text{ GHz} = \text{clock speed} = \frac{1}{\text{cycle time}} = \frac{1}{250 \text{ ps}}$$

 
# Sequential Circuits

---

- Until now, circuits were combinational – when inputs change, the outputs change after a while (time = logic delay thru circuit)




 - We want the clock to act like a start and stop signal – a “latch” is a storage device that separates these circuits – it ensures that the inputs to the circuit do not change during a clock cycle


 
# Sequential Circuits

- Sequential circuit: consists of combinational circuit and a storage element
- At the start of the clock cycle, the rising edge causes the “state” storage to store some input values



- This state will not change for an entire cycle (until next rising edge)
- The combinational circuit has some time to accept the value of “state” and “inputs” and produce “outputs”
- Some of the outputs (for example, the value of next “state”) may feed back (but through the latch so they’re only seen in the next cycle)